



FACULTY OF ENGINEERING
ELECTRONICS & ELECTRICAL
COMMUNICATIONS DEP.

Cairo University

Faculty of Engineering

Dept. of Electronics and Electrical Communications

Third Year

ELC-3060

Analog IC Design

Project

Universal Bi-quadratic Filter
(Parameters Design and Simulations)

Under Supervision of
Dr. Mohamed Mubarak
T.A. Ahmed Hassan

By
Email

Amir Ahmed Hassan
amir.mohamed01@eng-st.cu.edu.eg

Universal Biquadratic Filter

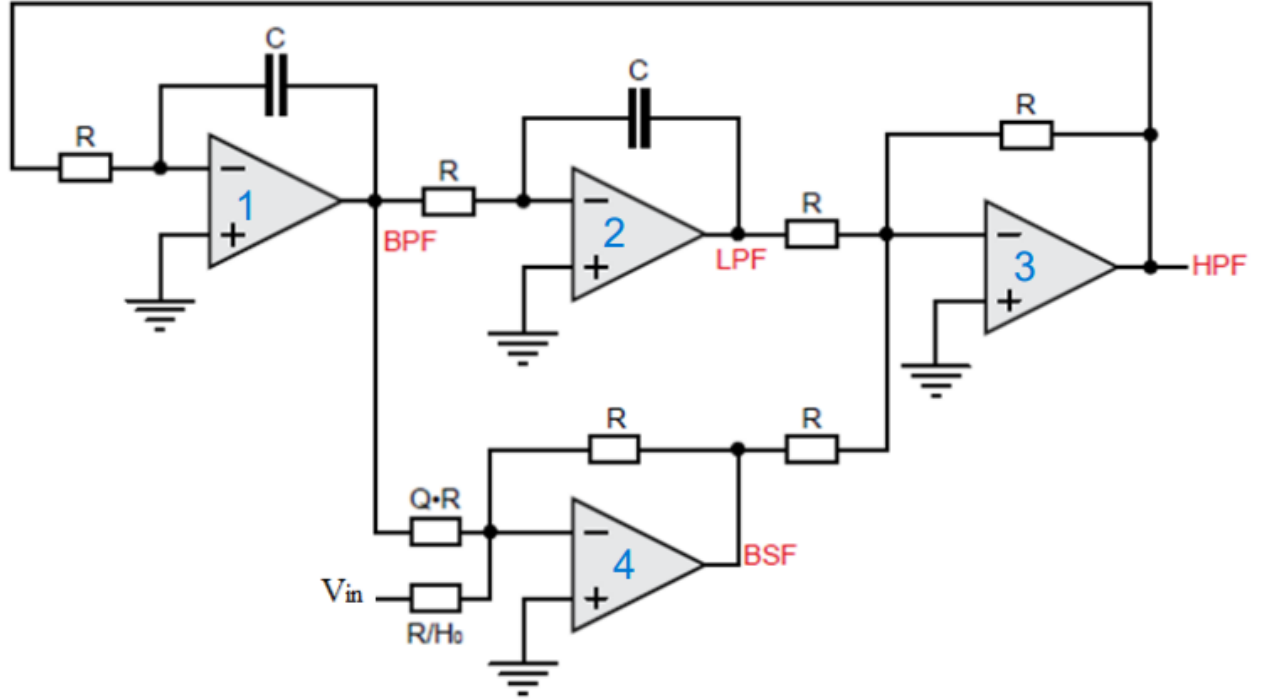


Figure 1: Circuit Diagram from the project statement, 1 numbered op-amps in blue to make Derivations

1- Derivation and Components Design.

Assume all op-amps are ideal and in negative feedback. Output of each op-amp is given as: $V_{out} = A_v (V_{in+} - V_{in-})$. Since the output is finite, While $A_v \rightarrow \infty$, then $(V_{in+} = V_{in-})$. We approach the derivation by doing KCL at input nodes using s-domain.

$$\text{KCL for op-amp 1: } \frac{V_{HPF}}{R} = -V_{BPF} (sC). \quad \therefore V_{HPF} = (-sCR) V_{BPF} \quad \rightarrow 1$$

$$\text{KCL for op-amp 2: } \frac{V_{BPF}}{R} = -V_{LPF} (sC). \quad \therefore V_{BPF} = (-sCR) V_{LPF} \quad \rightarrow 2$$

$$\text{KCL for op-amp 3: } \frac{V_{LPF}}{R} + \frac{V_{BSF}}{R} = \frac{-V_{HPF}}{R}. \quad \therefore V_{HPF} = -V_{LPF} - V_{BSF} \quad \rightarrow 3$$

$$\text{KCL for op-amp 4: } \frac{V_{in}}{R/H} + \frac{V_{BPF}}{R.Q} = \frac{-V_{BSF}}{R}. \quad \therefore H.V_{in} + \frac{1}{Q} V_{BPF} = -V_{BSF} \quad \rightarrow 4$$

$$\text{From 3, } -V_{BSF} = V_{HPF} + V_{LPF}, \text{ Substitute in 4.} \quad \therefore H.V_{in} + \frac{1}{Q} V_{BPF} = V_{HPF} + V_{LPF}$$

$$\text{From 2, } V_{BPF} = (-sCR) V_{LPF}, \quad \text{From 1,} \quad V_{HPF} = (-sCR) V_{BPF} = (sCR)^2 V_{LPF}$$

$$\text{Substitute to make the equation in terms of } V_{LPF} \quad \therefore H.V_{in} + \frac{-(sCR)}{Q} V_{LPF} = (sCR)^2 V_{LPF} + V_{LPF}$$

$$\therefore H.V_{in} = (s^2 C^2 R^2 + \frac{(sCR)}{Q} + 1) V_{LPF} \quad \therefore \frac{V_{LPF}}{V_{in}} = \frac{H}{s^2 C^2 R^2 + \frac{sCR}{Q} + 1} = \frac{\left(\frac{H}{C^2 R^2}\right)}{s^2 + \frac{s}{QRC} + \left(\frac{1}{C^2 R^2}\right)}$$

Now substitute in 2, $V_{BPF} = (-sCR) V_{LPF}$, $\therefore \frac{V_{BPF}}{V_{in}} = \frac{-H.(sCR)}{s^2 C^2 R^2 + \frac{sCR}{Q} + 1} = \frac{-H (\frac{s}{RC})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$

Now substitute in 1, $V_{HPF} = (-sCR) V_{BPF}$, $\therefore \frac{V_{HPF}}{V_{in}} = \frac{H. s^2 C^2 R^2}{s^2 C^2 R^2 + \frac{sCR}{Q} + 1} = \frac{H. s^2}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$

Now substitute in 4, $-V_{BSF} = V_{HPF} + V_{LPF}$, $\therefore \frac{V_{BSF}}{V_{in}} = \frac{-H. (s^2 C^2 R^2 + 1)}{s^2 C^2 R^2 + \frac{sCR}{Q} + 1} = \frac{-H. (s^2 + (\frac{1}{C^2 R^2}))}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$

Below is a list of transfer functions' standard forms of second order filters. The blue highlighted parameter represents an additional gain (and phase in case of negative sign) to the standard form:

$$H_{LPF}(s) = \frac{\omega_o^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)} \equiv \frac{H. (\frac{1}{C^2 R^2})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})} \quad H_{HPF}(s) = \frac{s^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)} \equiv \frac{H. s^2}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$$

$$H_{BPF}(s) = \frac{\frac{\omega_o}{Q}s}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)} \equiv \frac{-HQ (\frac{s}{QRC})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})} \quad H_{BSF}(s) = \frac{s^2 + \omega_o^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)} \equiv \frac{-H. (s^2 + (\frac{1}{C^2 R^2}))}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$$

Fast intuition on parameters:

H: DC gain (the frequency response should be shifted vertically upwards by $20 \log |H|$).

Q: Quality factor of filter, it can represent $(\frac{\omega_o}{BW})$ graphically.

ω_o : Cut-off frequency in rad/sec. $\omega_o = \frac{1}{RC}$.

Design required:

$$f_o = 1 \text{ MHz} \quad (\omega_o = 2\pi f_o = 6.283 \times 10^6 \text{ rad/sec}) \quad Q = 2.2 \quad H = 1$$

Using the cut-off frequency we get, $RC = 1/\omega_o = 1.59155 \times 10^{-7} \text{ sec}$. This is the Design Curve.

In IC design, component values get translated into area. Capacitance, $C = 1\text{fF}/\mu\text{m}^2$ and typically capacitor size ranges between 10 pF (100 $\mu\text{m} \times 100 \mu\text{m}$) to 100 fF (10 $\mu\text{m} \times 10 \mu\text{m}$). For resistor values, a huge resistor will increase thermal noise power level. $S(f) = 4KTR$. However, a small resistor will lead to high current and power consumption. Resistors are in kilo ohms typically.

The following figure shows our design space:

Green area: $1 \text{ k}\Omega < R < 100 \text{ k}\Omega$

Pink area: $1\text{fF} < C < 10 \text{ pF}$

Design point chosen A

$$C = 5.4 \text{ pF} \quad R = 29.4 \text{ k}\Omega$$

$$R/H = 29.4 \text{ k}\Omega \quad R*Q = 64.5 \text{ k}\Omega$$

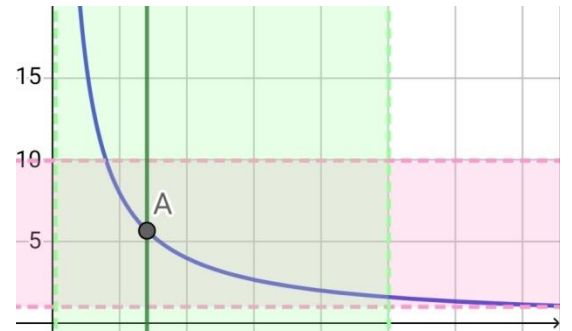


Figure 2: x-axis represents resistance in $\text{k}\Omega$
y-axis represents the Capacitance in pF

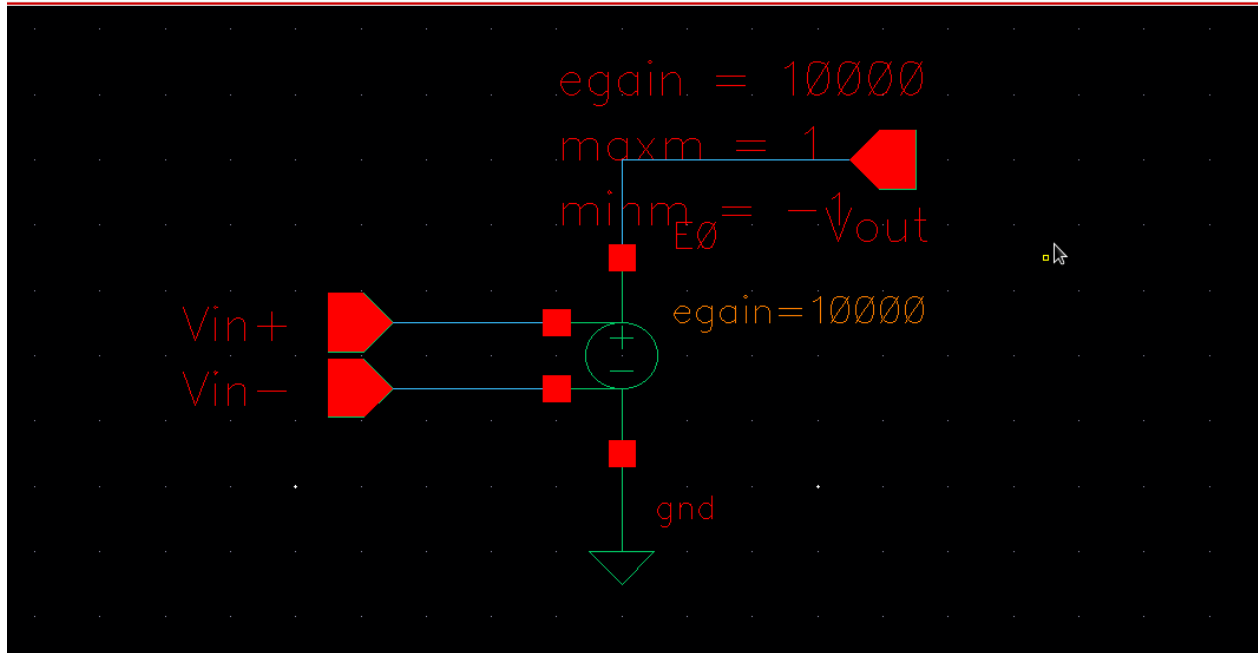


Figure: 3 Schematic of ideal op-amp

We modeled it as a voltage-controlled voltage source with volt gain = 10,000. And a maximum $|V_{out}| < 1$ volt. Note that we don't have any pole. Also we don't need a buffer stage. Because the resistance seen ($R_{out} = 0$). Volt source is modeled as a short circuit in small signal model.

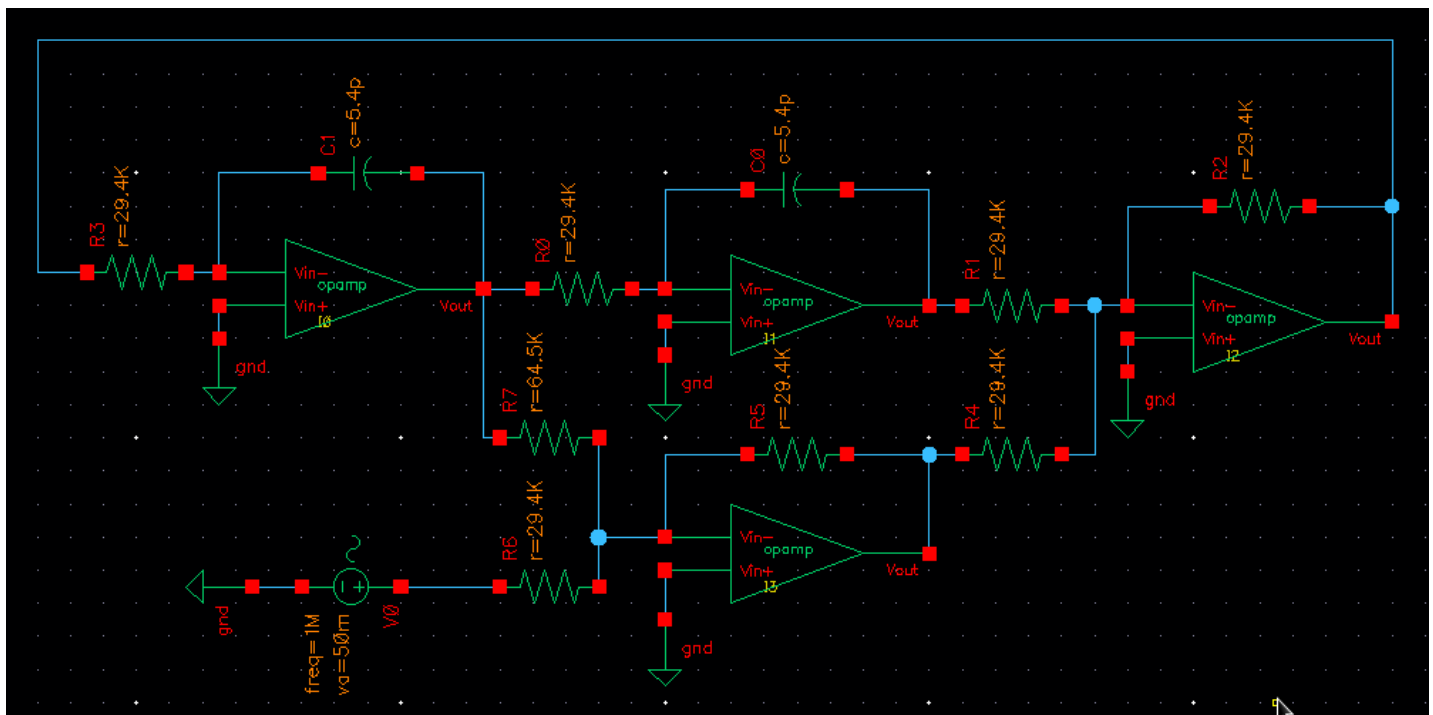


Figure: 4 Schematic of Biquadratic Filter with components values visible on schematic

2- Frequency Response.

2.1. Low Pass Filter Frequency Response: ($s = j\omega$)

$$H_{LPF}(s) = \frac{\omega_o^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}, \quad H_{LPF}(\omega) = \frac{\omega_o^2}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}, \quad |H_{LPF}(\omega)| = \frac{\omega_o^2}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}.$$

$$@(\omega \rightarrow 0) \quad \therefore |H_{LPF}(\omega)| = 1, \quad < \theta = 0^\circ$$

$$@(\omega \rightarrow \infty) \quad \therefore |H_{LPF}(\omega)| = 0, \quad < \theta = -180^\circ$$

$$@(\omega \rightarrow \omega_o) \quad \therefore H_{LPF}(\omega) = \frac{\omega_o^2}{j\frac{\omega_o^2}{Q}} = \frac{Q}{j}$$

$$\therefore |H_{LPF}(\omega_o)| = Q, \quad < \theta_{@ \omega_o} = -90^\circ$$

$$@(\omega \rightarrow \omega_{peak}), \text{ max magnitude} \quad \therefore \frac{d|H(\omega)|}{d\omega} = 0, \quad \therefore 2(\omega_o^2 - \omega^2)(-2\omega) + 2(\frac{\omega\omega_o}{Q})(\frac{\omega_o}{Q}) = 0$$

$$\text{Let } \omega \neq 0, \text{ then divide by } 2\omega \quad \therefore 2(\omega^2 - \omega_o^2) = -(\frac{\omega_o}{Q})^2 \quad \therefore \omega^2 = \omega_o^2(1 - \frac{1}{2Q^2})$$

$$\omega_{peak} = \omega_o \sqrt{1 - \frac{1}{2Q^2}} \quad \rightarrow \text{will give real value only if } Q > \frac{1}{\sqrt{2}}$$

$$|H_{LPF}(\omega_{peak})| = \frac{\omega_o^2}{\sqrt{(\omega_o^2 - \omega_{peak}^2)^2 + (\frac{\omega_{peak}\omega_o}{Q})^2}} = \frac{\omega_o^2}{\sqrt{\frac{\omega_o^4}{4Q^4} + \frac{\omega_o^4}{Q^2}(1 - \frac{1}{2Q^2})}} = \frac{Q^2}{\sqrt{Q^2 - \frac{1}{4}}} \text{ slightly } > Q$$

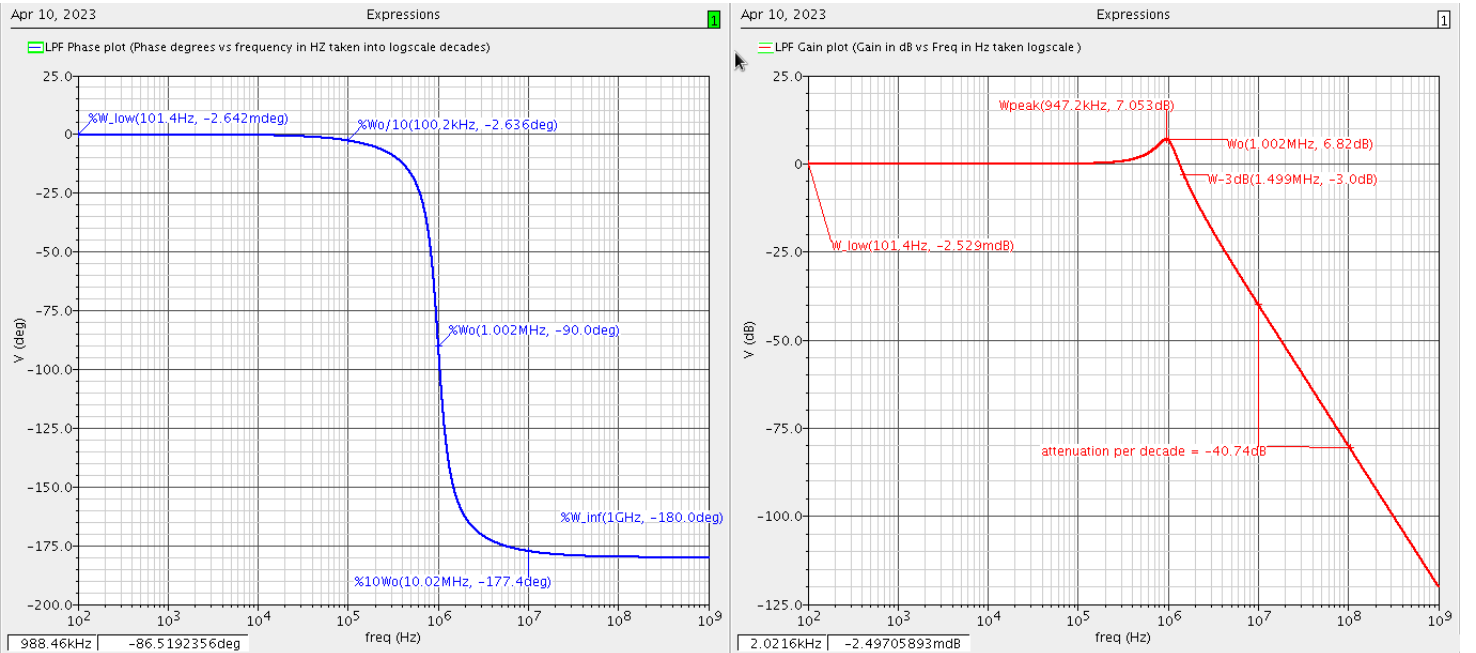


Figure 5: LPF frequency response: magnitude and phase plots

Now, let's compare the measured quantities vs. the theoretical quantities by derivations for LPF

	Measured at Cadence	Theoretically
Cut-off frequency (ω_o)	From phase plot At phase = -90° $f_o = 1.002$ MHz, by marker $\omega_o = 6.296 \times 10^6$ rad/sec	$C = 5.4$ pF $R = 29.4$ k Ω $Q = 2.194$ $H = 1$ $H_{LPF}(s) = \frac{H \cdot (\frac{1}{C^2 R^2})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})} = \frac{H \cdot \omega_o^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}$ $\omega_o = \frac{1}{RC} = 6.3 \times 10^6$ rad/sec $f_o = 1.0024$ MHz
DC Gain (H)	At low frequency, $ H_{LPF}(\omega_{low}) = 20 \log H $ $H = 0$ dB = 1	Defined as a design parameter (ratio between resistors) $H = \left(\frac{29.4 \text{ k}\Omega}{29.4 \text{ k}\Omega}\right) = 1$
Quality Factor (Q)	From magnitude plot @ ω_o , $ H_{LPF}(\omega_o) = Q = 6.82$ dB $Q = 6.82$ dB = 2.1928	Defined as a design parameter (ratio between resistors) $Q = \left(\frac{64.5 \text{ k}\Omega}{29.4 \text{ k}\Omega}\right) = 2.194$
Peaking Frequency (ω_{peak})	$f_{peak} = 947.2$ kHz, by marker $A_{peak} = 7.053$ dB, by marker $A_{peak} = 2.2524$	$f_{peak} = f_o \sqrt{1 - \frac{1}{2Q^2}} = 948.9$ kHz $A = Q^2 / \sqrt{Q^2 - \frac{1}{4}} = 2.2533$

2.2. High Pass Filter Frequency Response: ($s = j\omega$)

$$H_{HPF}(s) = \frac{s^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}, \quad H_{HPF}(\omega) = \frac{-\omega^2}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}, \quad |H_{HPF}(\omega)| = \frac{\omega^2}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}.$$

$$@(\omega \rightarrow 0) \quad \therefore |H_{HPF}(\omega)| = 0, \quad < \theta = 180^\circ \quad (\text{divide by } \omega^2 \text{ and take limits} = \frac{-1}{\infty})$$

$$@(\omega \rightarrow \infty) \quad \therefore |H_{HPF}(\omega)| = 1, \quad < \theta = 0^\circ$$

$$@(\omega \rightarrow \omega_o) \quad \therefore H_{HPF}(\omega) = \frac{-\omega_o^2}{j\frac{\omega_o^2}{Q}} = \frac{-Q}{j}$$

$$\omega_{peak} = \omega_o \sqrt{1 + \frac{1}{2Q^2}}$$

$$\therefore |H_{HPF}(\omega_o)| = Q, \quad < \theta_{@ \omega_o} = 90^\circ$$

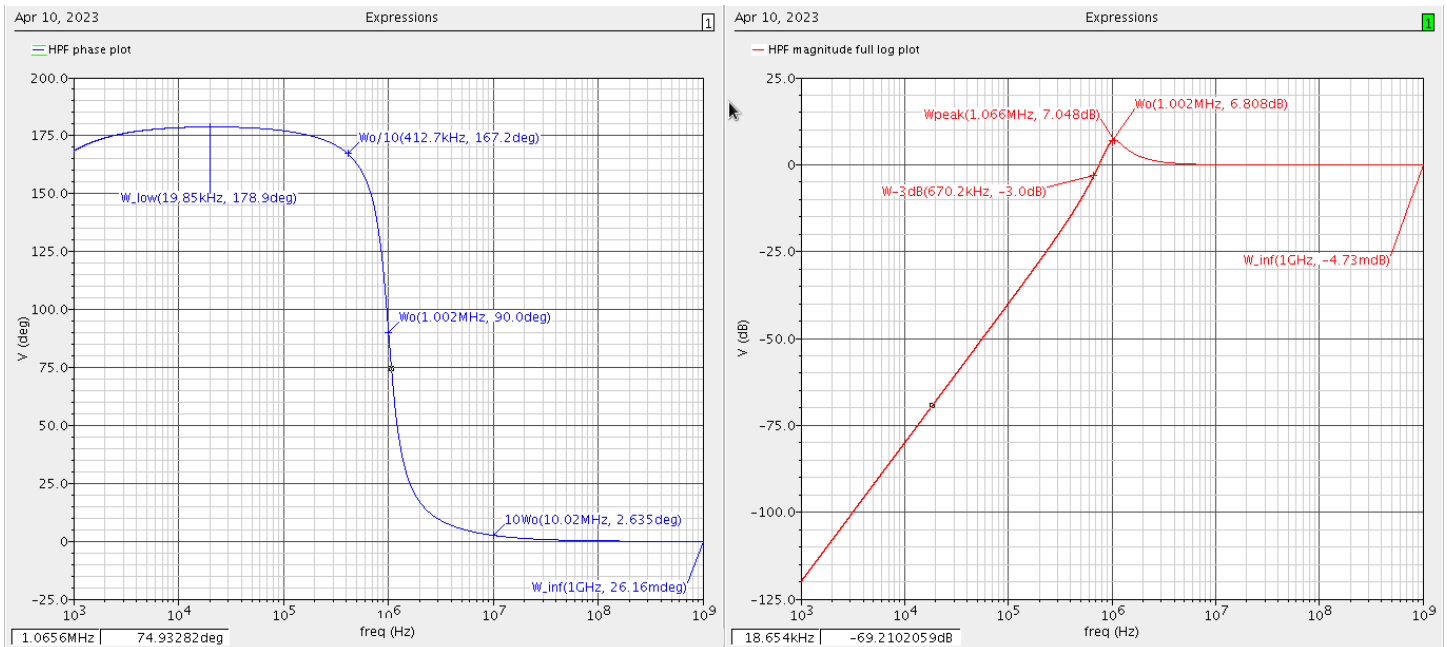


Figure 6: HPF frequency response: magnitude and phase plots

	Measured at Cadence	Theoretically
Cut-off frequency (ω_o)	From phase plot At phase = 90° $f_o = 1.002$ MHz, by marker $\omega_o = 6.296 \times 10^6$ rad/sec	$C = 5.4$ pF $R = 29.4$ k Ω $Q = 2.194$ $H = 1$ $H_{HPF}(s) = \frac{H.s^2}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})} = \frac{H.s^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}$ $\omega_o = \frac{1}{RC} = 6.3 \times 10^6$ rad/sec $f_o = 1.0024$ MHz
Gain (H)	At high frequency, $ H_{HPF}(\omega_{inf}) = 20 \log H $ $H = 0$ dB = 1	Defined as a design parameter (ratio between resistors) $H = \left(\frac{29.4 \text{ k}\Omega}{29.4 \text{ k}\Omega}\right) = 1$
Quality Factor (Q)	From magnitude plot @ ω_o , $ H_{HPF}(\omega_o) = Q = 6.808$ dB $Q = 6.808$ dB = 2.19	Defined as a design parameter (ratio between resistors) $Q = \left(\frac{64.5 \text{ k}\Omega}{29.4 \text{ k}\Omega}\right) = 2.194$

2.3. Band Pass Filter Frequency Response: ($s = j\omega$)

$$H_{BPF}(s) = \frac{\frac{\omega_o}{Q}s}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}, \quad H_{BPF}(\omega) = \frac{j \frac{\omega \omega_o}{Q}}{(\omega_o^2 - \omega^2) + j \frac{\omega \omega_o}{Q}}, \quad |H_{BPF}(\omega)| = \frac{\frac{\omega \omega_o}{Q}}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega \omega_o}{Q})^2}}.$$

$$@(\omega \rightarrow 0) \quad \therefore |H_{BPF}(\omega)| = 0, \quad < \theta = 90^\circ \quad (\text{divide by } \text{and take limits} = \frac{j}{\infty})$$

$$@(\omega \rightarrow \infty) \quad \therefore |H_{BPF}(\omega)| = 1, \quad < \theta = -90^\circ \quad (\text{take limits} = \frac{j}{-\infty})$$

$$@(\omega \rightarrow \omega_o) \quad \therefore H_{BPF}(\omega) = \frac{j \frac{\omega \omega_o}{Q}}{j \frac{\omega \omega_o}{Q}} = 1 \quad \therefore |H_{BPF}(\omega_o)| = 1, \quad < \theta_{@ \omega_o} = 0^\circ$$

$$@(\omega \rightarrow \omega_{1,2}, -3\text{dBs}) \quad \therefore |H_{BPF}(\omega)| = \frac{1}{\sqrt{2}} = \frac{\frac{\omega \omega_o}{Q}}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega \omega_o}{Q})^2}}. \quad (\text{Solve for BW and 3dBs})$$

$$2\left(\frac{\omega \omega_o}{Q}\right)^2 = (\omega_o^2 - \omega^2)^2 + \left(\frac{\omega \omega_o}{Q}\right)^2 \quad \therefore (\omega_o^2 - \omega^2)^2 = \left(\frac{\omega \omega_o}{Q}\right)^2 \quad (\text{accept only +ve freq})$$

$$\omega^2 + \frac{\omega \omega_o}{Q} - \omega_o^2 = 0 \quad \therefore \omega_{1,2} = \frac{\pm \frac{\omega_o}{Q} + \sqrt{(\frac{\omega_o}{Q})^2 + 4\omega_o^2}}{2} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \frac{1}{4Q^2}}$$

$$\therefore \text{BW} = \omega_2 - \omega_1 = \frac{\omega_o}{Q}$$

$$\therefore \omega_o^2 = \omega_2 \omega_1$$

Note that these standard derivations are for a function that looks like: $H_{BPF}(s) = \frac{\frac{\omega_o}{Q}s}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}$

our function looks like: $\frac{-H(\frac{s}{RC})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})} = \frac{-HQ(\frac{s}{QRC})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$. This affects derivations by:

Magnitude shifts up by $20 \log |QH| \cong 6.824$ dB; Phase shifts down by -180° .

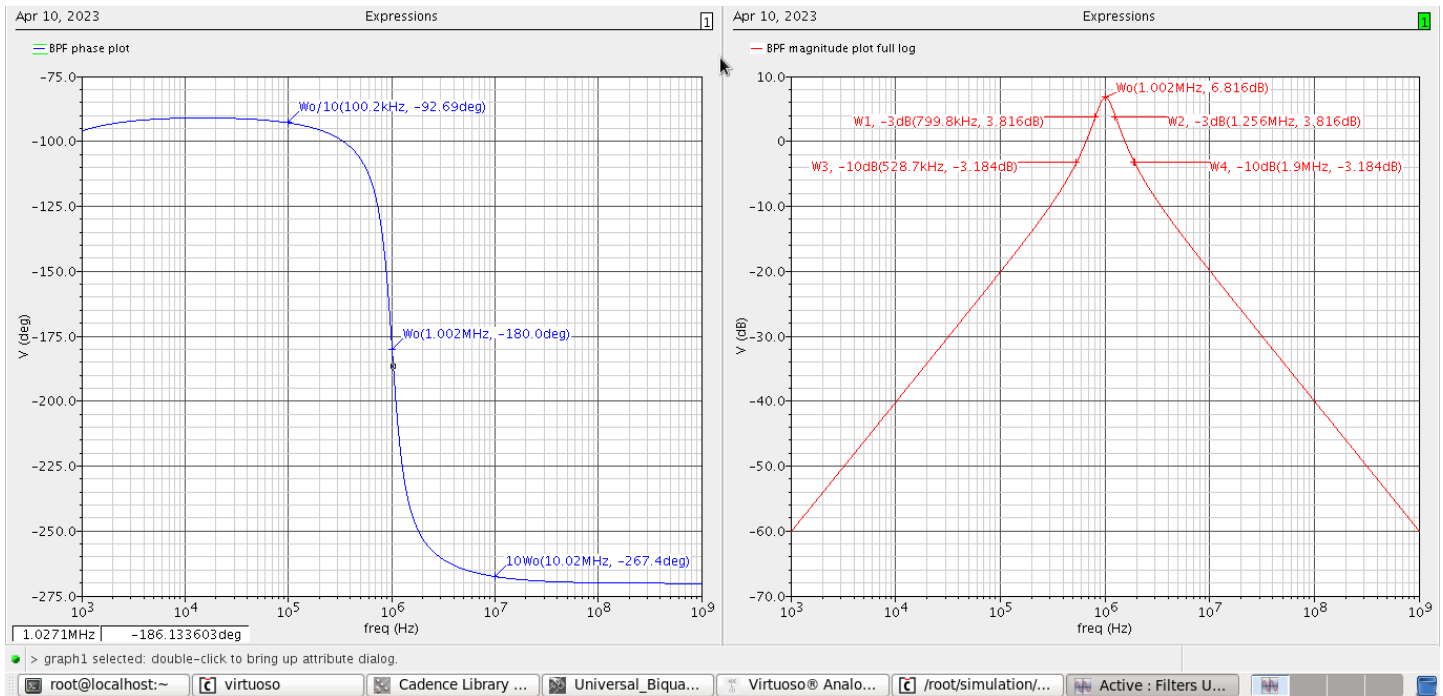


Figure 7: BPF frequency response: magnitude and phase plots

	Measured at Cadence	Theoretically
Cut-off frequency (ω_o)	From phase plot At phase = -180° $f_o = 1.002 \text{ MHz}$, by marker $\omega_o = 6.296 \times 10^6 \text{ rad/sec}$	$C = 5.4 \text{ pF}$ $R = 29.4 \text{ k}\Omega$ $Q = 2.194$ $H = 1$ $H_{BPF}(s) = \frac{-HQ \left(\frac{s}{QRC}\right)}{s^2 + \frac{s}{QRC} + \left(\frac{1}{C^2 R^2}\right)} = \frac{-HQ \left(\frac{\omega_o s}{Q}\right)}{(s^2 + \frac{\omega_o s}{Q} + \omega_o^2)}$ $\omega_o = \frac{1}{RC} = 6.3 \times 10^6 \text{ rad/sec}$ $f_o = 1.0024 \text{ MHz}$
3dB points $\omega_{1,2}$	$f_1 = 799.8 \text{ kHz}$ $f_2 = 1.256 \text{ MHz}$ Check: $\sqrt{f_1 f_2} = 1.00227 \text{ MHz}$	$\omega_{1,2} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \frac{1}{4Q^2}}$ $f_1 = 799.34 \text{ kHz}$ $f_2 = 1.256 \text{ MHz}$
Bandwidth BW	$BW = f_2 - f_1 = 456.2 \text{ kHz}$	$BW = f_2 - f_1 = \frac{f_o}{Q} = 456.7 \text{ kHz}$
Quality Factor (Q)	$BW = \frac{\omega_o}{Q}$ $Q = \frac{\omega_o}{BW} = \frac{1.002}{0.4562} = 2.196$	Defined as a design parameter (ratio between resistors) $Q = \left(\frac{64.5 \text{ k}\Omega}{29.4 \text{ k}\Omega}\right) = 2.194$
Gain (H) check on H and Q	From magnitude plot $ H_{BPF}(\omega_o) = HQ = 6.816 \text{ dB}$ $20 \log H + 20 \log Q = 6.816 \text{ dB}$ $20 \log H = -0.012 \text{ dB}$ $H = 1.001 \cong 1$ (note that the error in approx.. is due to Q, but H is 1)	Defined as a design parameter (ratio between resistors) $H = \left(\frac{29.4 \text{ k}\Omega}{29.4 \text{ k}\Omega}\right) = 1$

2.4. Band Stop Filter Frequency Response: (imaginary zeroes are used to create notch at ω_o)

$$H_{BSF}(s) = \frac{s^2 + \omega_o^2}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}, \quad H_{BSF}(\omega) = \frac{(\omega_o^2 - \omega^2)}{(\omega_o^2 - \omega^2) + j\frac{\omega\omega_o}{Q}}, \quad |H_{BSF}(\omega)| = \frac{(\omega_o^2 - \omega^2)}{\sqrt{(\omega_o^2 - \omega^2)^2 + (\frac{\omega\omega_o}{Q})^2}}.$$

$$@(\omega \rightarrow 0) \quad \therefore |H_{BSF}(\omega)| = 1, \quad < \theta = 0^\circ$$

$$@(\omega \rightarrow \infty) \quad \therefore |H_{BSF}(\omega)| = 1, \quad < \theta = 0^\circ$$

$$@(\omega \rightarrow \omega_o) \quad \therefore H_{BSF}(\omega) = 0, \quad \therefore |H_{BSF}(\omega_o)| = 0 = -\infty \text{ dB}, \quad < \theta_{@ \omega_o} = 0^\circ$$

$$@(\omega \rightarrow \omega_o^-) \quad \therefore H_{BSF}(\omega) = 0, \quad < \theta_{@ \omega_o^-} = -90^\circ \quad (\text{limits} = \frac{+1}{j \cdot \infty})$$

$$@(\omega \rightarrow \omega_o^+) \quad \therefore H_{BSF}(\omega) = 0, \quad < \theta_{@ \omega_o^+} = 90^\circ \quad (\text{limits} = \frac{-1}{j \cdot \infty})$$

Note that 3dB points $\omega_{1,2}$ are same derivation as in BPF

$$\therefore \omega_o^2 = \omega_2 \omega_1$$

$$\therefore \omega_{1,2} = \frac{\pm \frac{\omega_o}{Q} + \sqrt{(\frac{\omega_o}{Q})^2 + 4\omega_o^2}}{2} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \frac{1}{4Q^2}}$$

$$\therefore \text{BW} = \omega_2 - \omega_1 = \frac{\omega_o}{Q}$$

Our function looks like: $\frac{-H(s^2 + \frac{1}{C^2 R^2})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})}$. This affects derivations by -180° to all phases.

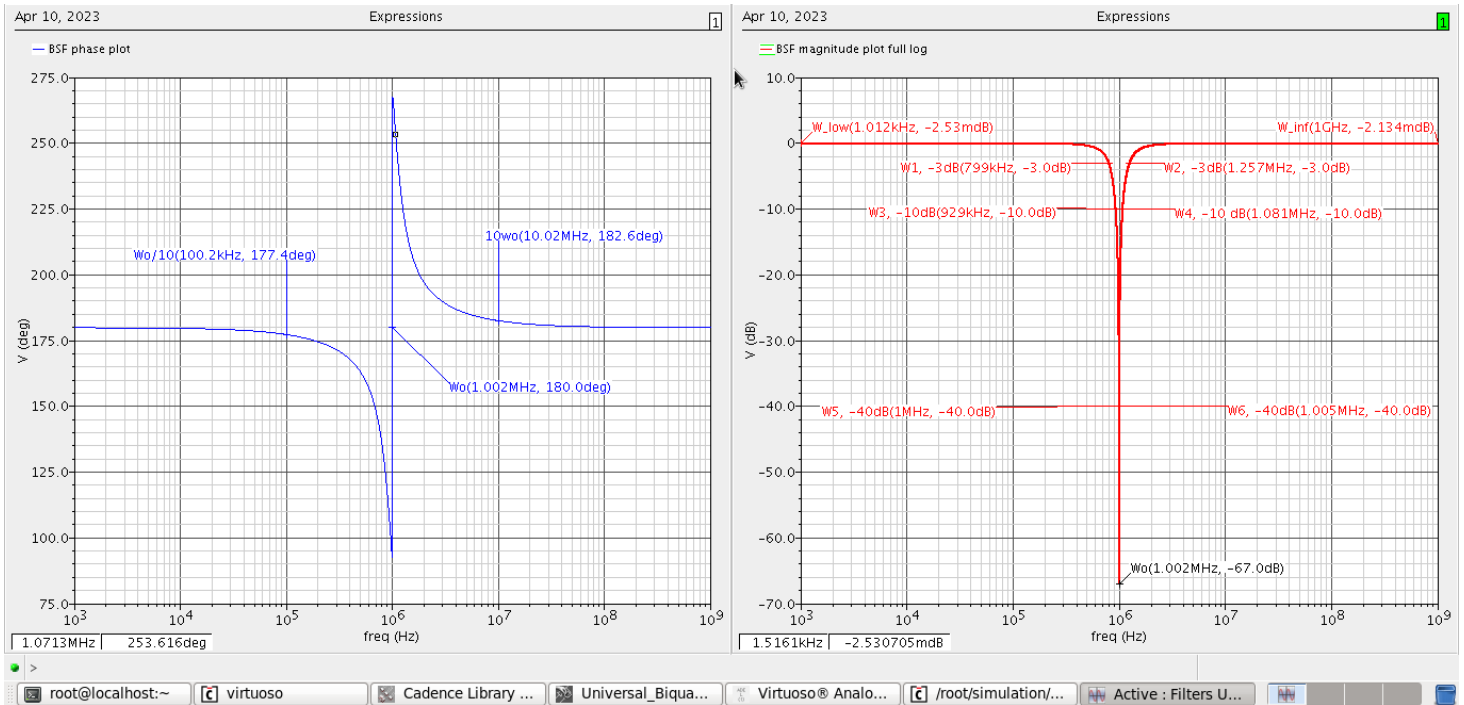


Figure 8: BSF frequency response: magnitude and phase plots

	Measured at Cadence	Theoretically
Cut-off frequency (ω_o)	From Magnitude Plot (notch) At Mag = -67 dB (ideally $-\infty$ dB) $f_o = 1.002$ MHz, by marker $\omega_o = 6.296 \times 10^6$ rad/sec	$C = 5.4$ pF $R = 29.4$ k Ω $Q = 2.194$ $H = 1$ $H_{BSF}(s) = \frac{-H(s^2 + \frac{1}{C^2 R^2})}{s^2 + \frac{s}{QRC} + (\frac{1}{C^2 R^2})} = \frac{-H.(s^2 + \omega_o^2)}{(s^2 + \frac{\omega_o}{Q}s + \omega_o^2)}$ $\omega_o = \frac{1}{RC} = 6.3 \times 10^6$ rad/sec $f_o = 1.0024$ MHz
3dB points $\omega_{1,2}$	$f_1 = 799$ kHz $f_2 = 1.257$ MHz Check: $\sqrt{f_1 f_2} = 1.00217$ MHz	$\omega_{1,2} = \pm \frac{\omega_o}{2Q} + \omega_o \sqrt{1 + \frac{1}{4Q^2}}$ $f_1 = 799.34$ kHz $f_2 = 1.256$ MHz
Bandwidth BW	$BW = f_2 - f_1 = 458$ kHz	$BW = f_2 - f_1 = \frac{f_o}{Q} = 456.7$ kHz
Quality Factor (Q)	$BW = \frac{\omega_o}{Q}$ $Q = \frac{\omega_o}{BW} = \frac{1.002}{0.458} = 2.188$	Defined as a design parameter (ratio between resistors) $Q = \left(\frac{64.5 \text{ k}\Omega}{29.4 \text{ k}\Omega} \right) = 2.194$
Gain (H) check on H and Q	From magnitude plot $ H_{BSF}(\omega_{low}) = H = 0$ dB $20 \log H = 0$ dB $H = 1$	Defined as a design parameter (ratio between resistors) $H = \left(\frac{29.4 \text{ k}\Omega}{29.4 \text{ k}\Omega} \right) = 1$

There are other definitions of BW like 10 dB bandwidth. Ideally the magnitude at notch is $-\infty$ dB. We can't get BW in terms of (notch rejection + x dB) in this example.

3- Transient Analysis. (Sine Wave)

Using “Vsin” with following specs:

Amplitude = 100 mV (to avoid output voltage clipping)

Frequency = 1 MHz ($f = f_o$) $\rightarrow V_{out} = V_{in} * H(\omega_o)$

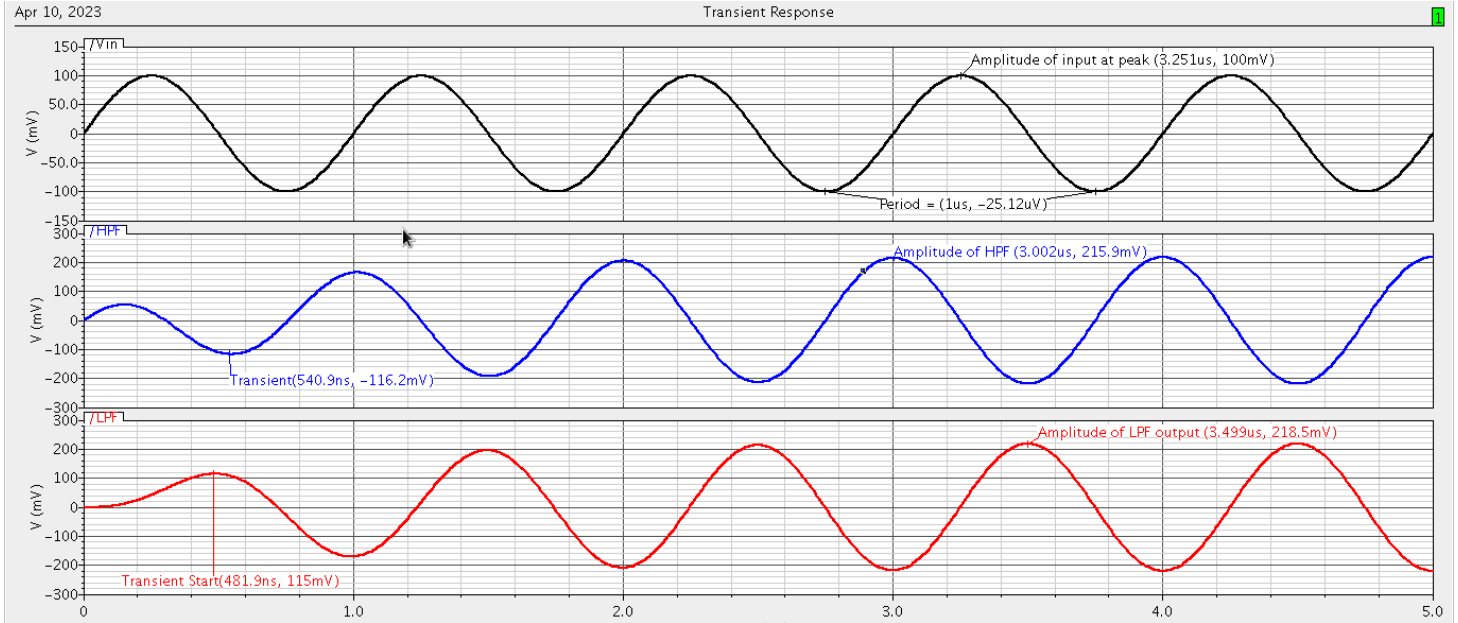


Figure 9: Transient analysis due to sine wave: LPF and HPF outputs

	Measured at Cadence	Theoretically
Amplitudes	$V_{in} = 100 \text{ mV}$ $V_{LPF} = 218.5 \text{ mV}$ $V_{HPF} = 215.9 \text{ mV}$ at steady state values approach $220 \text{ mV} = Q * 100 \text{ mV}$	$\therefore H_{HPF}(\omega_o) = Q$ $\therefore H_{LPF}(\omega_o) = Q$ $Q = 2.194$ $V_{LPF} = 219.4 \text{ mV (Amplitude)}$ $V_{HPF} = 219.4 \text{ mV (Amplitude)}$
Delay (Phase Shift)	V_{HPF} and V_{LPF} are 180° out of phase V_{HPF} peak at $3.002 \text{ } \mu\text{sec}$ V_{in} peak at $3.251 \text{ } \mu\text{sec}$ V_{LPF} peak at $3.499 \text{ } \mu\text{sec}$ $T = 1 \text{ } \mu\text{sec} = \lambda = 360^\circ$. Then if: $\Delta T_{peak} = 0.25 \text{ } \mu\text{sec} = \frac{\lambda}{4} = 90^\circ$ difference in phase $\Delta T_{peak} = 0.5 \text{ } \mu\text{sec} = \frac{\lambda}{2} = 180^\circ$ difference in phase V_{HPF} leads V_{in} by 90° , V_{LPF} lags V_{in} by 90° V_{HPF} leads V_{LPF} by 180°	$\therefore H_{HPF}(\omega_o) = Q, < \theta_{@ \omega_o} = 90^\circ$ $\therefore H_{LPF}(\omega_o) = Q, < \theta_{@ \omega_o} = -90^\circ$ $V_{HPF} = Q V_{in} < 90^\circ$ $V_{LPF} = Q V_{in} < -90^\circ$ There is 180° phase difference between V_{HPF} and V_{LPF}

4- Transient Analysis. (Pulse Wave).

Using “Vpulse” with following specs

V1 (V_High) = 100 mv (to avoid output voltage clipping),

V2 (V_Low) = 0 v

Frequency = 1 MHz ($f = f_o$)

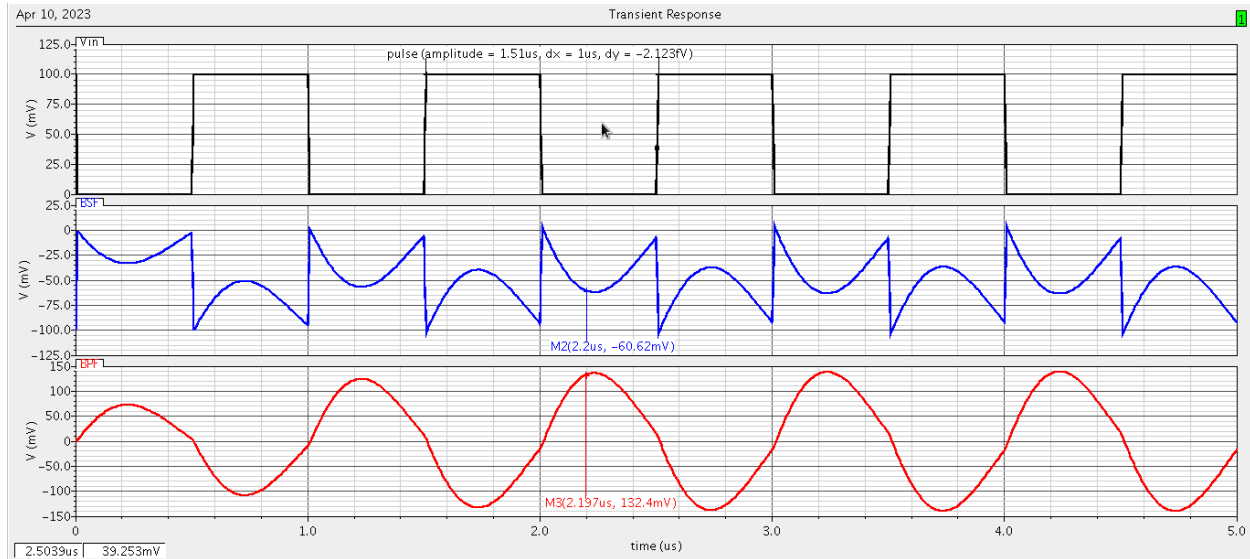


Figure 10: Transient analysis due to Pulse wave: BPF and BSF outputs

Square Pulse can be analyzed using Fourier Coefficients. We use the trigonometric Fourier:

$$a_o = \frac{\text{Area}}{T} = 50 \text{ mV (DC component)} \quad b_n = 0 \text{ (even signal)}$$

$$a_n = \frac{2}{T} \int_{-T/2}^{T/2} f(t) \sin(n\omega_o t) dt = \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \quad (\text{Only gives value for odd } n)$$

$$V_{in}(t) = 100 \text{ mv} \left[\frac{1}{2} + \sum \frac{2}{n\pi} \sin\left(\frac{n\pi}{2}\right) \cos(n\omega_o t) \right] \rightarrow \text{Fourier synthesis of Square Wave}$$

$$V_{in}(t) = 100 \text{ mv} \left[\frac{1}{2} + \frac{2}{\pi} (\cos(\omega_o t) - \frac{1}{3} \cos(3\omega_o t) + \frac{1}{5} \cos(5\omega_o t) - \dots) \right]$$

$$V_{out}(t) =$$

$$100 \text{ mv} \left[\frac{1}{2} H(0) + \frac{2}{\pi} (\cos(\omega_o t) H(\omega_o) - \frac{1}{3} \cos(3\omega_o t) H(3\omega_o) + \frac{1}{5} \cos(5\omega_o t) H(5\omega_o) - \dots) \right]$$

This means frequency components pass, get amplified, or get rejected.

@DC ($\omega = 0$)	$H_{BPF}(0) = 0$ (rejection)	$H_{BSF}(0) = 1$ (pass)
@ ω_o	$H_{BPF}(\omega_o) = Q$ (amplified and pass)	$H_{BSF}(\omega_o) = 0$ (rejection/blocked)
@ $3\omega_o$	$H_{BPF}(3\omega_o) \rightarrow$ rejection by some dB	$H_{BSF}(3\omega_o) = 1$ (pass)
@ $5\omega_o, \dots$	All higher harmonics are rejected	All higher harmonics pass as well
	f_o component passes, others rejected	All components pass except f_o .

Conclusions:

We notice that BPF signal is like a sine wave (slightly distorted sine wave). This is because the BPF amplified the component which is exactly at $f = f_o$, Then all other harmonics faced high rejection ratio.

On the other hand the BSF has blocked the frequency component at its notch $f = f_o$. Yet it allowed all other components to pass without rejection. So its output appears as if we subtracted a sine wave (point by point subtraction) from the rectangular pulse.

DFT analysis of output waveforms:

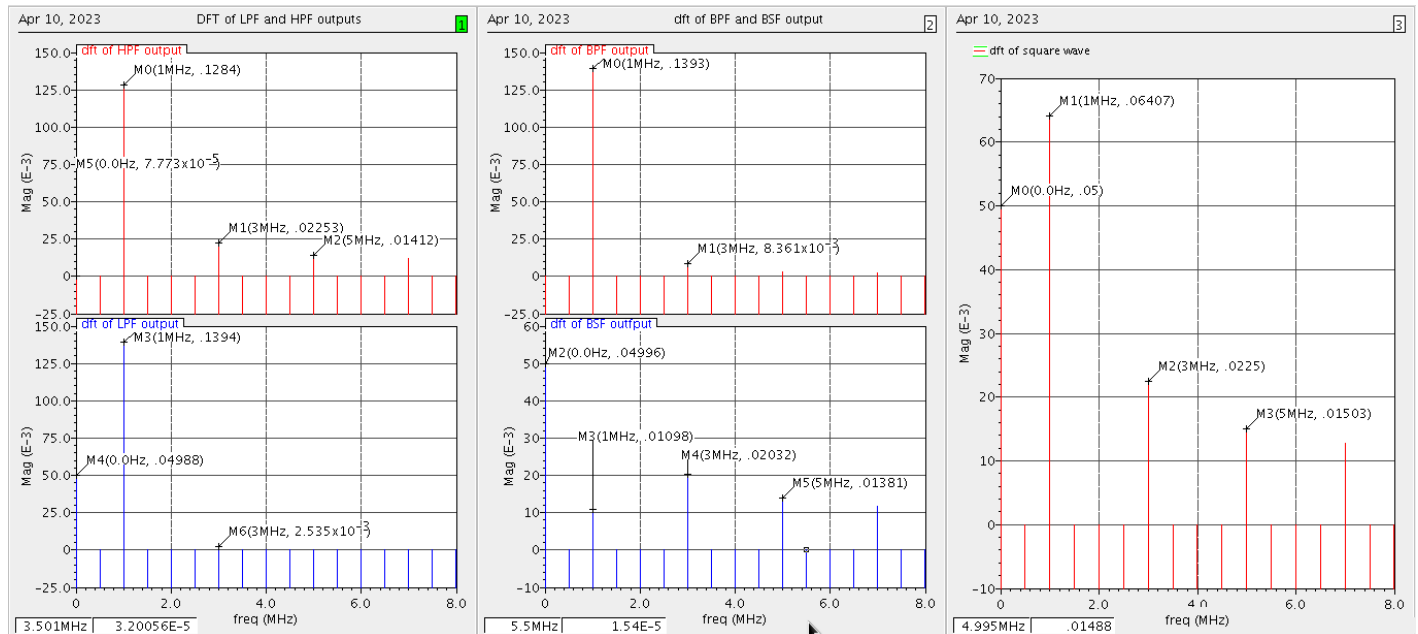


Figure 11: DFT analysis BPF and BSF outputs

Comment:

DFT verifies the Fourier coefficients of rectangle wave. For BPF, highest component is at 1MHz (f_o) while higher harmonics get rejected. For BSF, All components pass nearly without rejection except the component at the notch (f_o).